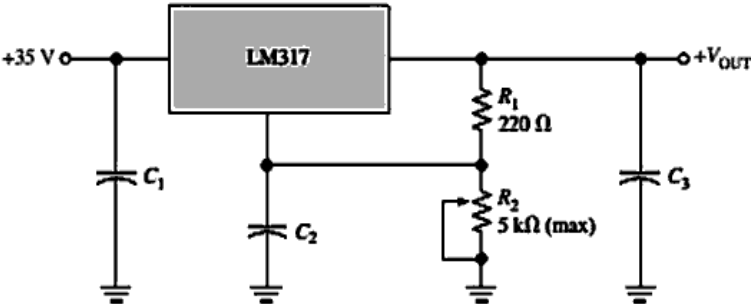


C)	Determine the minimum and maximum output voltages for the voltage regulator in the following Figure. Assume $I_{ADJ} = 50 \mu A$. ($R_1=220\Omega$ and $R_2=5K\Omega$).	3/CO4	6
			
Q. 5	Solve Any Two of the following.		12
A)	Define transducer. Explain the working principle and constructional details of Thermistor.	1&2/CO5	6
B)	Explain the working of LDR with neat diagram. state its advantages and applications.	2/CO5	6
C)	Explain with the help of circuit diagram, working of LVDT.	2/CO5	6
*** End ***			

The grid and the borders of the table will be hidden before final printing.